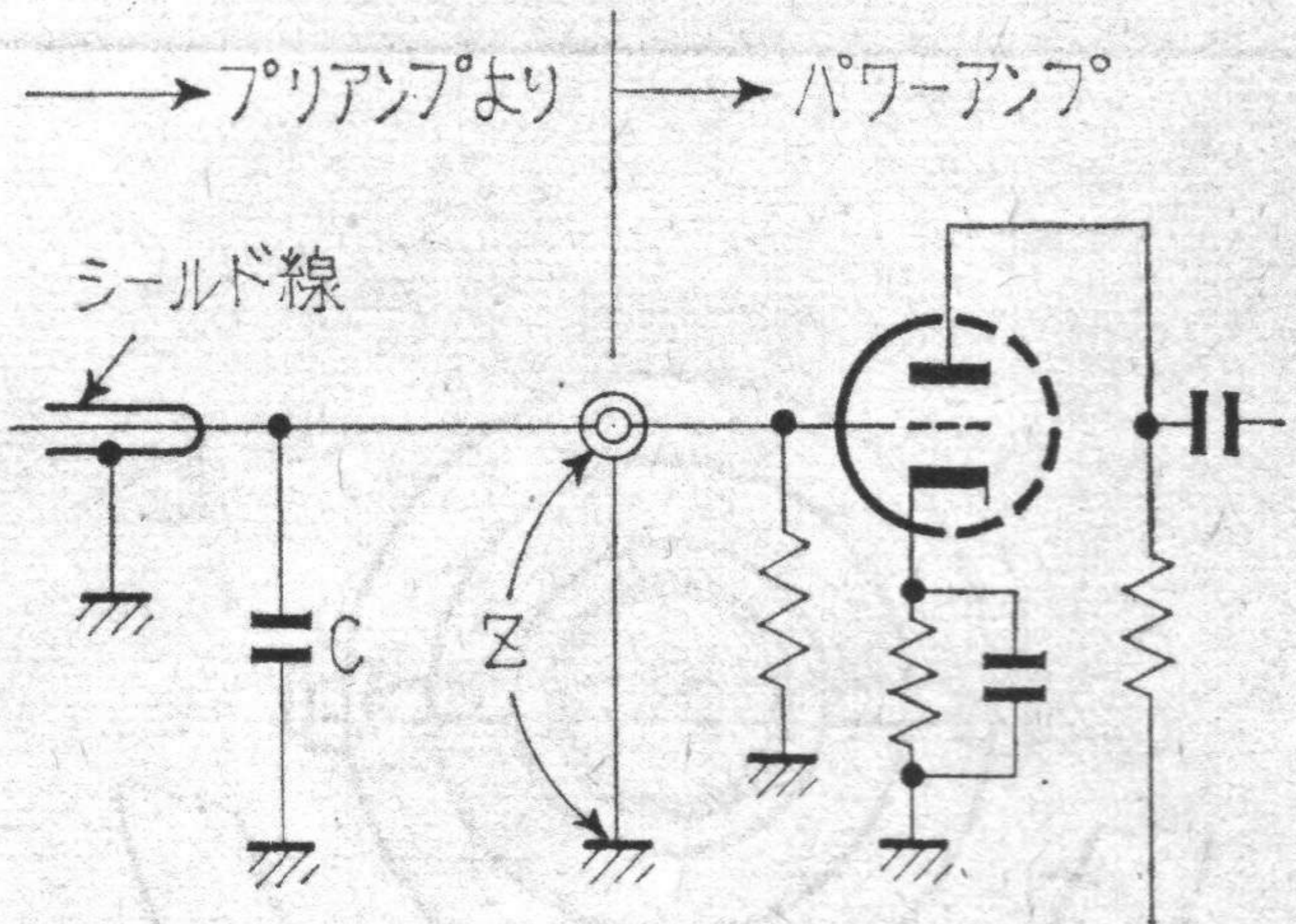


[第5図]



$$\begin{cases} C = 470 \text{ pF} \\ Z = 330 \text{ k}\Omega \end{cases}$$

$$f_c = \frac{1}{2\pi RC}$$

$$= \frac{1}{(2 \times 3.14) \times (330 \times 10^3) \times (470 \times 10^{-12})}$$

$$= 1026 \text{ (Hz)}$$